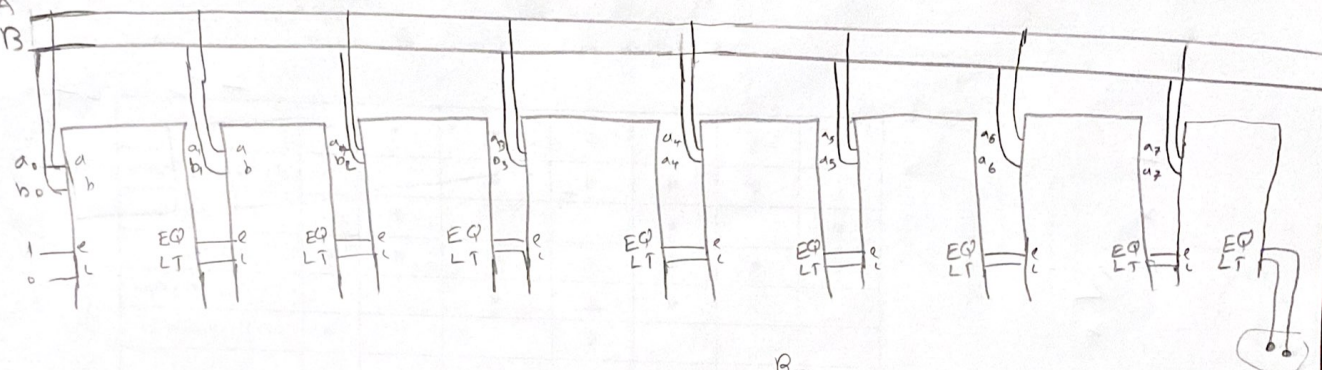


Worksheet 810198519


2



we have 169 ns delay for transmission $B = 00000000 \rightarrow 10000000$
 $A = 00000000$
 we have 158 ns delay for transmission $A = 00000000 \rightarrow 10000000$
 $B = 10000000$

final result

(3)

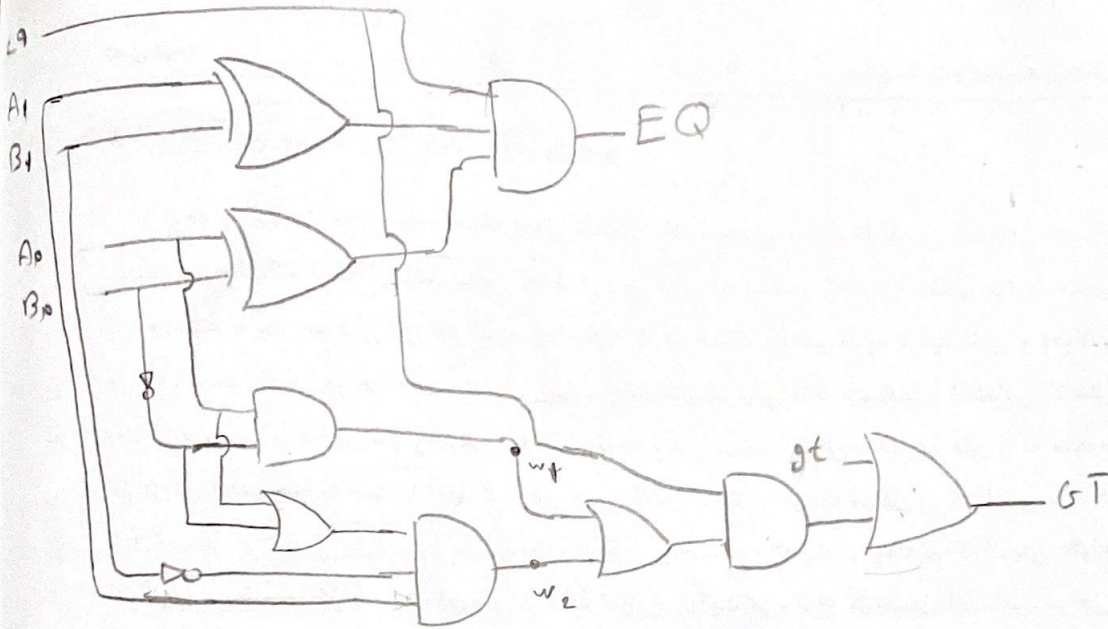

EQ:

Worst case delay T_{01} :
$$\begin{matrix} 3\text{-input AND} \\ T_{01} \end{matrix} 17 + \begin{matrix} XOR \\ T_{01} \end{matrix} 12 = 29$$

Worst case delay T_{00} :
$$\begin{matrix} 3\text{-input AND} \\ T_{00} \end{matrix} 22 + \begin{matrix} XOR \\ T_{00} \end{matrix} 12 = 34$$

GT:

T_{01} :
$$\begin{matrix} OR \\ 19 \end{matrix} + \begin{matrix} AND \\ 13 \end{matrix} + \begin{matrix} OR \\ 19 \end{matrix} \rightarrow \begin{matrix} w_1=0 \rightarrow AND \\ 17 \end{matrix} \Rightarrow A_0=0$$

T_{00} :
$$\begin{matrix} OR \\ 17 \end{matrix} + \begin{matrix} AND \\ 17 \end{matrix} + \begin{matrix} OR \\ 17 \end{matrix} \rightarrow \begin{matrix} w_1=0 \rightarrow 3\text{-input AND} \\ 22 \end{matrix} + \begin{matrix} OR \\ 17 \end{matrix} + \begin{matrix} inverter T_{00} \\ 7 \end{matrix} = 97$$


we have 368 ns delay when this transmission occurs:

$A = 00000000 \rightarrow 10000000$
 $B = 00000000$

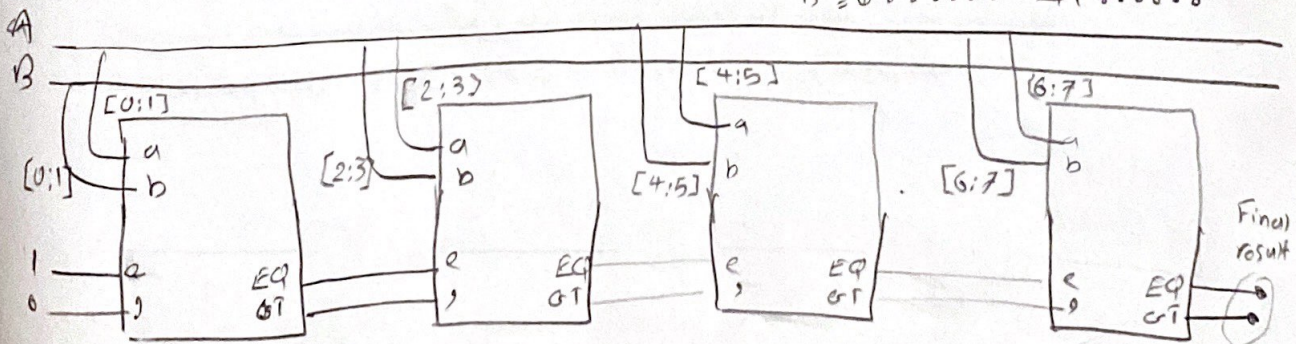(4)

we have 388 ns delay when this transmission occurs

$A = 10000000$
 $B = 00000000 \rightarrow 10000000$



disadvantages of TCS: we needed to implement it again (5)
like other gates such as 3-input NAND
and bigger delay value for small numbers

advantages of TCS: in bigger nums and more significant
bits, TCS is better than BCS
less-gates overall for delay